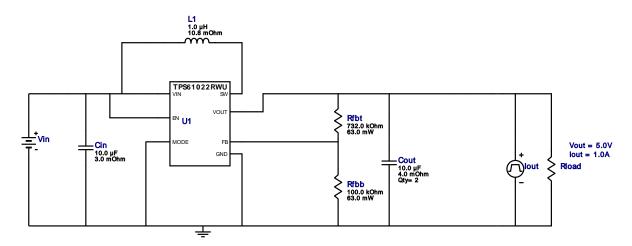


WEBENCH® Design Report

VinMin = 3.0V VinMax = 3.0V Vout = 5.0V lout = 1.0A Device = TPS61022RWUR Topology = Boost\_PassThrough Created = 2019-11-10 03:06:44.629 BOM Cost = \$1.59 BOM Count = 7 Total Pd = 0.24W

Design: 57 TPS61022RWUR TPS61022RWUR 3V-3V to 5.00V @ 1A




#### **Design Alerts**


#### **Component Selection Information**


1. The TPS61022 Device will operate in Pass-Through mode when Vin is greater than Vout. In Pass-Through mode, Vout is not regulated to the set Vout, instead Vout is Vin with the drop across the FET?s on-resistance and the DCR of the inductor. 2. This is a Boost Converter with 0.5V ultra-low input voltage. 3. The efficiency validation is done only for FPWM mode. Charts may be inaccurate for AutoMode at light loads and hence they are disabled for light loads.

# **Electrical BOM**

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cin	Kemet	C0805C106K8PACTU Series= X5R	Cap= 10.0 uF ESR= 3.0 mOhm VDC= 10.0 V IRMS= 11.43 A	1	\$0.03	0805 7 mm <sup>2</sup>
Cout	MuRata	GRM21BR71A106KE51L Series= X7R	Cap= 10.0 uF ESR= 4.0 mOhm VDC= 10.0 V IRMS= 4.35 A	2	\$0.14	0805 7 mm <sup>2</sup>
L1	Coilcraft	XFL4020-102MEB	L= 1.0 μH 10.8 mOhm	1	\$0.61	XFL4020 25 mm <sup>2</sup>
Rfbb	Vishay-Dale	CRCW0402100KFKED Series= CRCWe3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
Rfbt	Vishay-Dale	CRCW0402732KFKED Series= CRCWe3	Res= 732.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
U1	Texas Instruments	TPS61022RWUR	Switcher	1	\$0.65	RWU0007A 9 mm²

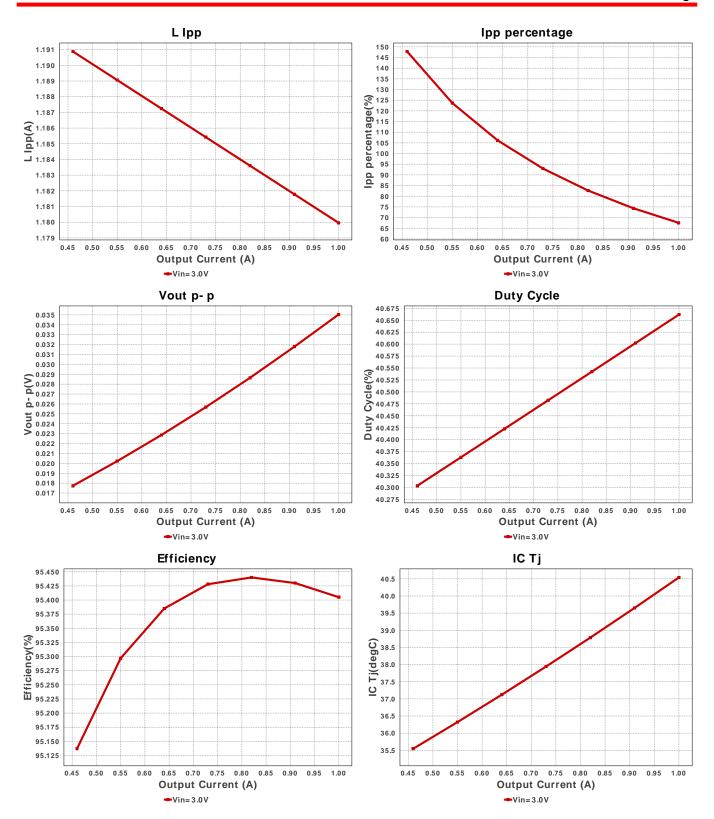

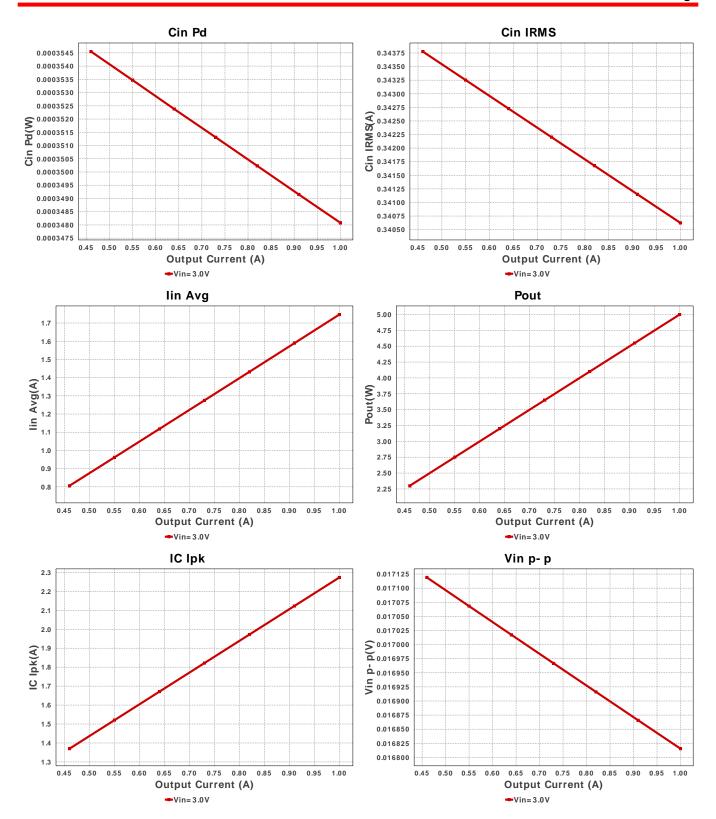

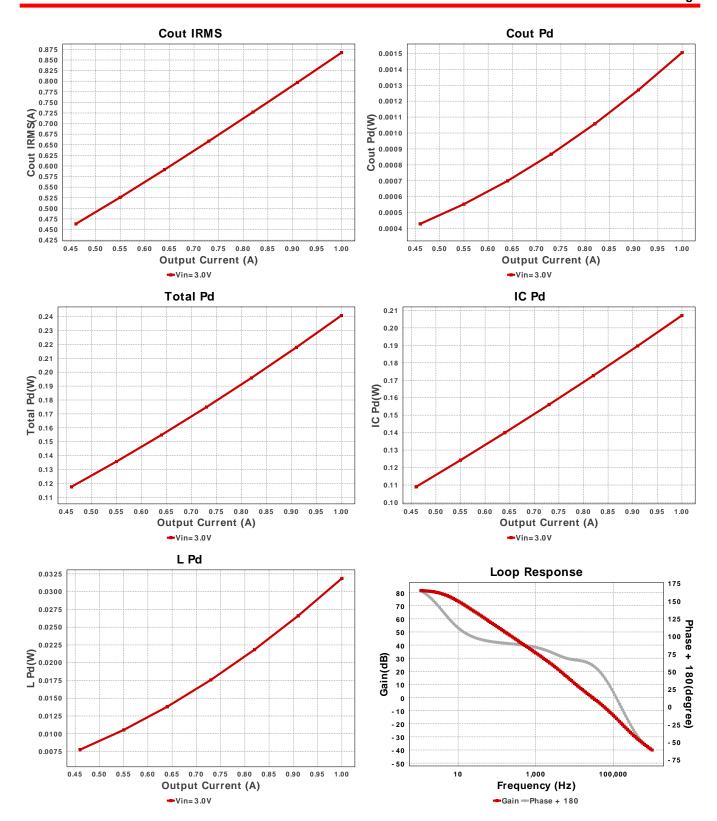

## **Operating Values**

#	Name	Value	Category	Description
1.	Cin IRMS	340.626 mA	Capacitor	Input capacitor RMS ripple current
2.	Cin Pd	348.08 μW	Capacitor	Input capacitor power dissipation
3.	Cout IRMS	867.576 mA	Capacitor	Output capacitor RMS ripple current
4.	Cout Pd	1.505 mW	Capacitor	Output capacitor power dissipation
5.	IC lpk	2.273 A	IC	Peak switch current in IC
6.	IC Pd	207.08 mW	IC	IC power dissipation
7.	IC Tj	40.54 degC	IC	IC junction temperature
8.	IC Tolerance	15.0 mV	IC	IC Feedback Tolerance
9.	ICThetaJA	50.9 degC/W	IC	IC junction-to-ambient thermal resistance
10.	lin Avg	1.747 A	IC	Average input current

#	Name	Value	Category	Description
11.	lpp percentage	67.544 %	Inductor	Inductor ripple current percentage (with respect to average inducto current)
12.	L lpp	1.18 A	Inductor	Peak-to-peak inductor ripple current
13.	L Pd	31.863 mW	Inductor	Inductor power dissipation
14.	Cin Pd	348.08 µW	Power	Input capacitor power dissipation
15.	Cout Pd	1.505 mW	Power	Output capacitor power dissipation
16.	IC Pd	207.08 mW	Power	IC power dissipation
17.	L Pd	31.863 mW	Power	Inductor power dissipation
18.	Total Pd	240.81 mW	Power	Total Power Dissipation
19.	BOM Count	7	System	Total Design BOM count
			Information	•
20.	Cross Freq	29.003 kHz	System	Bode plot crossover frequency
	•		Information	
21.	Duty Cycle	40.662 %	System	Duty cycle
	, ,		Information	, ,
22.	Efficiency	95.405 %	System	Steady state efficiency
	,		Information	· · · · · · · · · · · · · · · · · · ·
23.	FootPrint	60.0 mm <sup>2</sup>	System	Total Foot Print Area of BOM components
		00.0 111111	Information	
24.	Frequency	1.016 MHz	System	Switching frequency
			Information	g q,
25.	Gain Marg	-19.601 dB	System	Bode Plot Gain Margin
-0.	Can marg	10.001 42	Information	2000 Flot Gaill Margin
26.	lout	1.0 A	System	lout operating point
_0.	lout	1.071	Information	Tout operating point
27.	Low Freg Gain	81.533 dB	System	Gain at 1Hz
	Low Freq Cam	01.000 dB	Information	Call at 1112
28.	Mode	CCM	System	Conduction Mode
20.	WOOC	OOW	Information	Conduction Wood
29.	Phase Marg	59.472 deg	System	Bode Plot Phase Margin
29.	i nase marg	39.472 deg	Information	bode i lot i liase margin
30.	Pout	5.0 W	System	Total output power
30.	Foul	3.0 W	Information	Total output power
31.	Total BOM	\$1.59	System	Total BOM Cost
) I.	Total BOW	φ1.59	Information	Total Bow Cost
32.	Vin	3.0 V	System	Vin operating point
<i>3</i> 2.	VIII	3.0 V	Information	viii operating point
33.	Vin n n	16.815 mV	System	Peak-to-peak input voltage
55.	Vin p-p	VIII C1 0.01	•	reak-to-peak iliput voitage
2.4	Vout	F 0 \/	Information	Operational Output Valtege
34.	Vout	5.0 V	System	Operational Output Voltage
) E	Vout Actual	4.002.17	Information	Vous Actual coloulated based on colouted visitance divides a section
35.	Vout Actual	4.992 V	System	Vout Actual calculated based on selected voltage divider resistors
20	Vant Talans	4 200 07	Information	Vest Televane hand on IC Televane (as less) and a life in
36.	Vout Tolerance	4.322 %	System	Vout Tolerance based on IC Tolerance (no load) and voltage divide
			Information	resistors if applicable
37.	Vout p-p	35.039 mV	System	Peak-to-peak output ripple voltage

## **Design Inputs**

Name	Value	Description	
lout	1.0	Maximum Output Current	
VinMax	3.0	Maximum input voltage	
VinMin	3.0	Minimum input voltage	
Vout	5.0	Output Voltage	
base_pn	TPS61022	Base Product Number	
source	DC	Input Source Type	
Та	30.0	Ambient temperature	

# WEBENCH® Assembly

#### Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of Cin and Cout, and the inductance and DC resistance of L1 before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

#### Soldering Component to Board

If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab town to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

#### Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 3.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to Vin and GND. Connect a digital volt meter and a load if needed to set the minimum lout of the design from Vout and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

#### Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between Vin and GND, a load is connected between Vout and GND and a current meter is connected in series between Vout and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.




# **WEBENCH®** Electrical Simulation Report

Design Id = 57


sim\_id = 1

Simulation Type = Input Transient

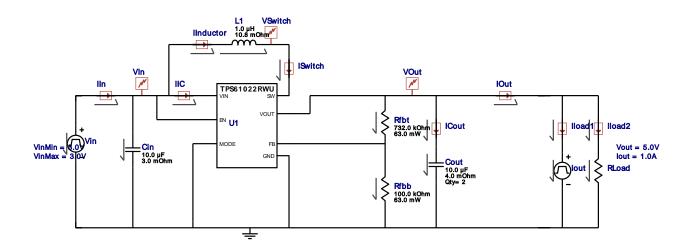

#### Simulation Parameters

#	Name	Parameter Name	Description	Values
1.	lout	signal_type I1 I2 Td Tr	Signal Type Initial Load Current Minimum Load Current Initial Time Delay Rise Time	PULSE 0 A 0.0 A 200u sec 1u sec
2.	RI oad	R	Load Resistance	5.0 ohm

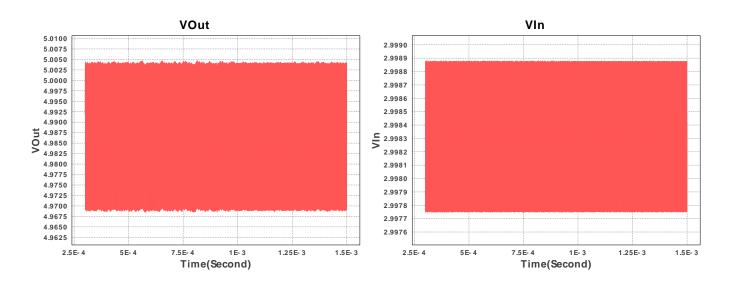

#### **Design Assistance**

- 1. Feature Highlights: 1. Device will operate in Pass-Through mode when Vin is greater than Vout. In Pass-Through mode, Vout is not regulated to the set Vout, instead Vout is Vin with the drop across the FET?s on-resistance and the DCR of the inductor. 2. Device will operate in PassThrough Mode When Vin is greater than Vout
- 2. Master key: B331BB6DC89D8D2D[v1]
- 3. TPS61022 Product Folder: http://www.ti.com/product/TPS61022: contains the data sheet and other resources.

#### Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.